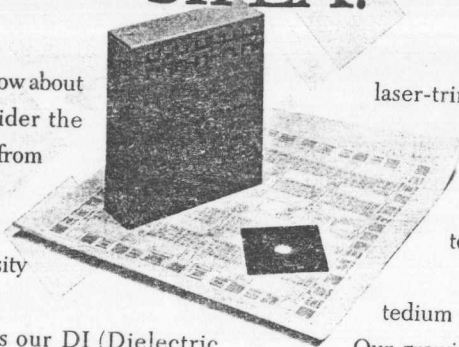


# THREE VAST IMPROVEMENTS IN ANALOG ASICS: SPEED, PRECISION, AND SIPEX.

Forget everything you know about analog ASICs and consider the performance you'll gain from our DataLinear Division's new SP1104 analog array: speed, precision, and density all in one chip.

The SP1104 uses our DI (Dielectric Isolation) process, so you can forget about parasitic junction-isolation effects like latch-up. You can also forget about the design limitations imposed by low performance PNPs. Our SP1104 uses full-complementary, high-bandwidth, vertical NPN ( $F_T \approx 1$  GHz) and PNP ( $F_T \approx 600$  MHz) transistors, both without collector-connection restrictions.

And forget about the problems of temperature tracking and precision. Our SP1104 uses low temperature-coefficient (100 ppm/°C), nichrome, thin-film resistors and they're even



laser-trimmable, down to .01% ratio matching, for that extra measure of precision. All this with a max voltage up to 35V.

And forget about the tedium of transistor-level designing. Our growing macro-cell library already includes op-amps, comparators, references, and transimpedance amplifiers. And finally, forget about another expensive software investment. We interface with industry-standard simulation packages, like P-SPICE and H-SPICE, and our layout package can run on any GDS II compatible workstation.

For a detailed description of the SP1104 and a copy of our 1988 product catalog, call 1-800-272-1772. In Massachusetts, call (508) 663-7811. Or write Sipex Corporation, DataLinear Division, 491 Fairview Way, Milpitas, CA 95035.

**Sipex** DataLinear  
Corporation Division

SIGNAL PROCESSING EXCELLENCE

CIRCLE NO 72

EDN January 19, 1989



op-amp feedback  
circuits  
Part 1

## Feedback plots offer insight into operational amplifiers

*Many engineers will benefit from a discussion of feedback effects and the construction of feedback plots for operational amplifiers. Part 1 of this series limits its discussion to single-stage amplifiers. Part 2 will conclude with an examination of multistage and composite amplifiers.*

Jerald G Graeme, Burr-Brown Corp

Feedback plots simplify the analysis of an op amp's closed-loop ac performance by showing bandwidth and stability conditions as a function of the op amp's gain and phase response. These plots also provide insight into noise performance and the special feedback requirements of circuits such as integrating converters and photodiode amplifiers.

Engineers routinely use Bode plots (Ref 1) to determine the bandwidth and frequency stability of voltage-gain op-amp circuits. A Bode plot provides a visual representation of an op amp's transfer response and its potential stability. Moreover, such plots define the circuit's pole and zero locations at the intercepts of the response-curve extensions.

The Bode plot of Fig 1, for example, shows the interaction of the magnitude response of the open-loop gain ( $A$ ) and the reciprocal of the feedback factor ( $1/\beta$ ).

The fraction of the output that feeds back to the input is  $\beta$ . The voltage-divider action of Fig 1's feedback network determines the value of  $\beta$ ; for moderate resistance values,  $\beta = R_1/(R_1 + R_2)$ . For this noninverting example, the feedback equation,  $A_{CL} = A/(1 + A\beta)$ , defines the closed-loop voltage gain.  $A\beta$  is the loop gain, and where it is high:

$$A_{CL} \approx 1/\beta = (R_1 + R_2)/R_1.$$

$A\beta$  represents the amplifier gain available to maintain the ideal closed-loop response. At the point where the loop gain no longer matches the feedback demand, the closed-loop curve deviates from the ideal. The Bode plot graphically defines this limit by plotting the  $1/\beta$  curve with the gain-magnitude response curve of the op amp. Because the  $1/\beta$  line represents the feedback demand, closed-loop requirements will be satisfied as long as this line is below the amplifier-gain curve. Where this condition is no longer true, the actual response drops, following the amplifier's open-loop response downward. The rate of descent for the roll-off is  $-20$  dB/decade (for most op amps) and is characteristic of a single-pole response. In Fig 1, the heavier line on the gain-magnitude plot depicts the resulting closed-loop curve.

### Back to basics

For a basic voltage-gain amplifier, the location of the  $f_p$  pole determines the closed-loop bandwidth. In this case, a single-pole roll-off determines the point at



Bode plots add a visual presentation of the op amp's transfer response and provide information on gain, phase, and noise characteristics.

which the gain magnitude goes below 3 dB (equivalent to 0.707 of its low-frequency level). To find this point relative to the Bode plots, rewrite the closed-loop gain as

$$A_{CL} = (1/\beta) / (1/A\beta + 1).$$

The bandwidth-defining gain error is a result of the  $1/A\beta$  term in the denominator. Because  $\beta$  is constant for the circuit in Fig 1, the amplifier gain ( $A$ ) determines the frequency dependence of the loop gain. For a typical op amp, the gain-bandwidth product is constant after the first break frequency occurs and when

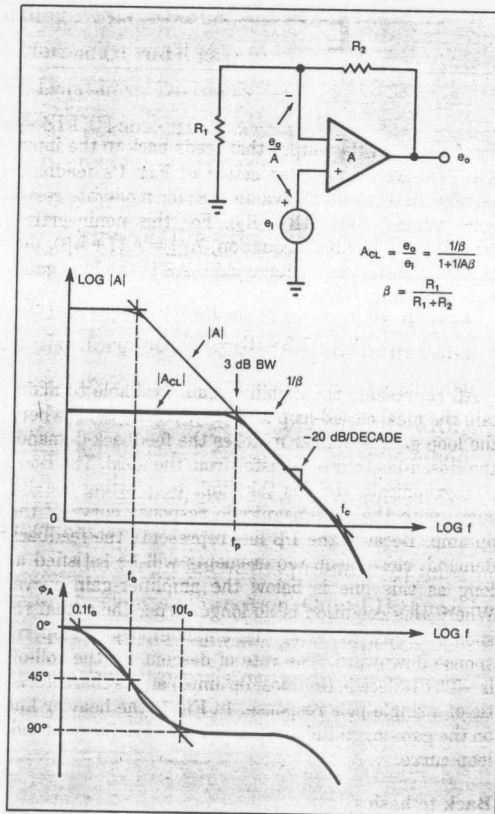


Fig 1—This feedback analysis provides a summary of loop conditions in the  $1/\beta$  curve and defines the underlying poles, zeros, and phase shift.

$A \approx jf_c/f = j|A|$  and where  $f_c$  is the amplifier's unity-gain crossover frequency. For this common condition,

$$A_{CL} = (1/\beta) / (1 + 1/(j|A|\beta)).$$

The bandwidth is defined in terms of the absolute value (magnitude) of  $A_{CL}$ :

$$|A_{CL}| = (1/\beta) / \sqrt{1 + (1/(|A|^2\beta^2))},$$

which, at the -3-dB point, becomes

$$|A_{CL}| = 0.707(1/\beta) = (1/\beta) / \sqrt{2}$$

Comparing the last two expressions, you can see that the -3-dB bandwidth occurs when  $|A| = 1/\beta$ . This equality is true when the gain supply drops to the exact level of the feedback demand. When you plot these two functions on the same graph, they reach equality at the intersection of the two curves. This intercept pinpoints the closed-loop pole location and defines the circuit bandwidth for the voltage-gain amplifier.

#### When it comes to stability

This critical intercept point also exhibits other characteristics that can help you define conditions for frequency stability. By relating the phase shift to the slopes of the gain-magnitude and  $1/\beta$  curves, you can determine the loop phase shift at this intercept. Again, the importance of the intercept is apparent from the closed-loop-gain expression,  $A_{CL} = A/(1 + A\beta)$ . If  $A\beta$  becomes -1, the closed-loop gain will be infinite and will support an output signal even in the absence of an input signal, which is a condition for oscillation. The magnitude of  $A\beta$  is unity only at the intercept point because it is at this point that  $A = 1/\beta$ ; a negative polarity for  $A\beta$  only requires 180° phase shift.

Virtually every practical analog circuit is a minimum-phase system. For such systems, which have only left-half-plane poles and zeros, you can directly read the phase shift from the gain-magnitude response (Ref 2). Although many op amps do have a right-plane zero caused by Miller phase compensation, the effects of this zero are suppressed below the unity-gain crossover. For the case of a minimum-phase system, a pole creates a -20-dB/decade response roll-off and a -90° phase shift; a zero produces the same effects but with opposite polarities. Additional poles and zeros simply add to the response slope and phase shift in increments of the same magnitude.

Relying on the feedback phase shift's correlation with the response slope, you can determine its value at the critical intercept from the gain-magnitude and  $1/\beta$  curves. For the example of Fig 1, the gain-magnitude curve has a slope of -20 dB/decade and the  $1/\beta$  curve has a zero slope for a net 90° feedback phase shift at the intercept. This situation leaves a phase margin of 90° out of the 180° that is needed to cause oscillation. Because the intercept is well removed from the open-loop-response break frequencies, the analysis of this example is easier to understand. The intercept occurs after the amplifier's first pole develops the full 90° phase shift, but well before the second pole has any effect.

#### Maximum error is 5.7°

In cases where the intercept is less than two decades from a response break, the Bode approximation of the phase shift shows a linear slope that has a maximum error of 5.7° (Ref 1). For Fig 1, the phase-shift approximation starts at 0° one decade before the break frequency  $f_c$ . From there, it increases linearly on the log scale to 45° at the break frequency and then to 90° one decade above it.

Using this approximation, you can combine the stability criteria for loop-gain magnitude and feedback phase shift to obtain the rate-of-closure indicator. Rather than computing phase shifts from slopes, you can use this indicator to deal with the slopes directly. Rate-of-closure is simply the difference in slopes of the gain-magnitude curve and the  $1/\beta$  curve when they intercept. This difference reflects the combined phase shift around the feedback loop. For Fig 1, the rate-of-closure is 20 dB/decade, which corresponds to a stable 90° phase shift.

In other cases, the slope of the  $1/\beta$  curve is not zero, giving a 40-dB/decade rate-of-closure that indicates an oscillatory 180° of phase shift. Rate-of-closure alone is an exact stability indicator where the intercept is at least two decades away from all other break frequencies. In still other cases, the Bode phase approximation modifies the rate-of-closure result.

#### Feedback network needs its independence

To use feedback relationships to perform circuit analysis, you should consider the feedback network separately. This separation parallels the nature of the op amp's open-loop gain, which is a characteristic of the amplifier in the absence of the feedback network. You only need to retain the loading effects between the amplifier and the feedback network to determine their individual responses (Ref 2). Then, by putting the two responses on the same plot, you can see how they will work together.

Fig 2 shows a generalized feedback condition defined by  $Z_1$  and  $Z_2$ . The equations of Fig 2a directly determine the circuit response for high loop gain and moderate impedances. Nonetheless, the input impedance of the amplifier alters the simplified results of these equations by shunting the feedback network. The inclusion of this loading effect on the feedback network completes the  $1/\beta$  analysis in the circuit of Fig 2b. Here, the op-amp input resistance ( $R_i$ ), differential input capacitance ( $C_{id}$ ), and common-mode input capacitance ( $C_{icm}$ ) all shunt impedance  $Z_1$ . Except for conditions where the feedback impedances have low values, you need to include these amplifier characteristics in your analysis.

Where there is impedance in series with the amplifier's noninverting input, you must add this too—along

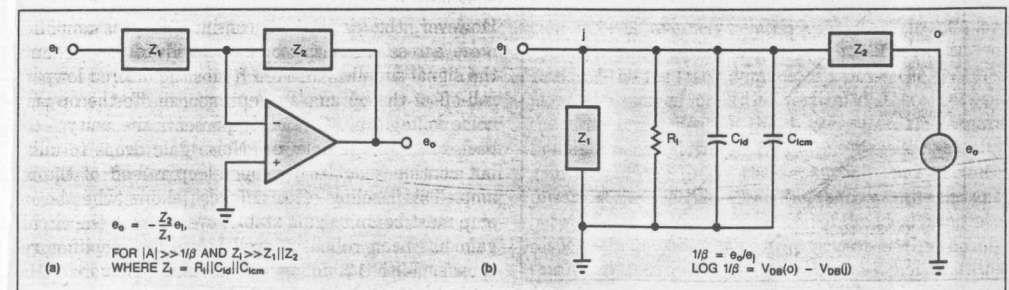


Fig 2—To determine the  $1/\beta$  curve for the generalized circuit of a, you can draw a voltage-divider circuit that represents the feedback network and the shunting effects of the amplifier input (b).



*The feedback network's voltage-divider action determines the feedback factor, which interacts with the open-loop gain to generate the overall circuit response.*

with the shunting effect of the input's  $C_{iem}$  capacitance. You can then find the feedback factor from the divider action,  $e_i/e_o$ . For the  $1/\beta$  curve, this result is inverted and, in the logarithmic format of computer simulations, becomes simply  $VDB(o) - VDB(j)$ . By adding this curve to the plot of the amplifier's gain-magnitude response, you can display the characteristics of the critical intercept for subsequent feedback interpretation.

#### Gain departures deserve consideration

The  $1/\beta$  curve also communicates performance information across the entire response range of the op amp. For example, it displays loop gain, which provides an indication of gain accuracy vs frequency and the ultimate bandwidth limit. Furthermore, the  $1/\beta$  curve demonstrates that the circuit's signal bandwidth can be different from its noise bandwidth. Note that the previous feedback-network analysis returns  $Z_1$  to

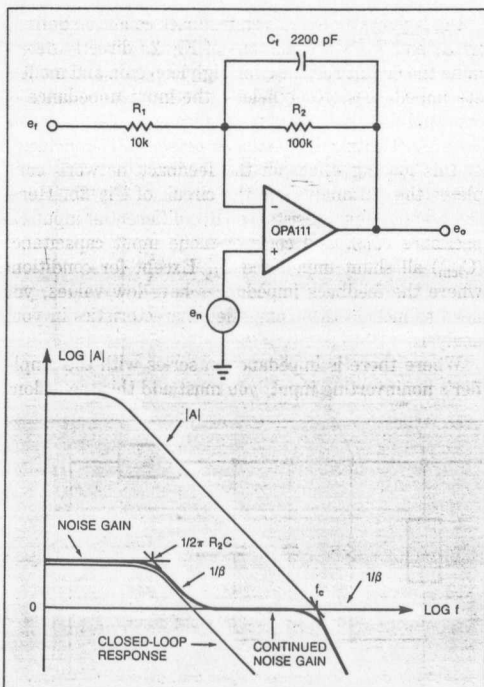


Fig 3—Highlighting the difference between closed-loop gain and noise gain, this inverting op-amp configuration demonstrates the greater bandwidth that is often available to amplifier noise.

ground as it would in a noninverting op-amp configuration, even though the op amp shown is in the inverting mode.

Underlying the difference between noise and signal bandwidth is the concept of noise gain, which is the source of some of the more common op-amp application problems. For any given feedback network, the inverting and noninverting configurations develop signal gains that differ in magnitude as well as in sign; nevertheless, the feedback conditions remain the same. In both cases, your feedback analysis is concerned with the gain-error voltage developed between the op-amp inputs. This error signal always receives the gain of the noninverting connection, as you would see if you performed superposition analysis. Superposition of the signal between the amplifier inputs grounds the signal source, producing the noninverting configuration.

The same condition holds true for the input voltage noise of an op amp, resulting in the noise-gain characteristic for the  $1/\beta$  curve. In practice, the noise gain and the  $1/\beta$  curve are the same—until they intercept with the gain-magnitude curve. After that, the noise gain rolls off with the amplifier open-loop response but the  $1/\beta$  curve continues on its path. For the noninverting voltage amplifier, the noise gain and the closed-loop gain,  $A_{CL}$ , are the same.

#### Watch out for surprises

In inverting configurations, this correspondence does not hold true, giving rise to frequent surprises during attempts at noise filtering. The simplest case of the inverting amplifier, where it is common practice to bypass the feedback resistor, serves to illustrate the inverting relationship (Fig 3). Bypassing the feedback resistor is intended to limit noise bandwidth, and it does indeed remove noise presented as an input signal. However, the circuit will continue to pass amplifier noise across the entire op-amp bandwidth.  $C_f$  shunts the signal supplied through  $R_1$  for the desired lowpass roll-off of the op amp's  $e_o/e_i$  response. To the op-amp noise voltage,  $e_n$ ,  $C_f$  merely presents the unity feedback of a voltage-follower. Noise gain drops to unity but continues out to the open-loop roll-off of the op amp. This leveling off of  $1/\beta$  also shows why the op amp must be unity-gain stable, even though the circuit gain has been rolled off well below the amplifier response. With  $1/\beta$  following the unity gain axis, the critical intercept occurs at  $f_c$ .

While the continued noise gain is at a lower level, it covers much of the amplifier bandwidth, which can

result in a dramatic increase in output noise. For example, if you're using the 2-MHz Burr-Brown OPA111 shown and choose  $C_f$  to obtain a 2-kHz roll-off, only 0.1% of the amplifier bandwidth will be enclosed in the intended system response. Although the logarithmic scale of the frequency axis may be visually deceptive, the remaining 99.9% of the bandwidth is still available to the amplifier's voltage noise. For an initial gain of 10, the output noise that this amplifier produces is more than doubled by the bandwidth effect. Many active-filter configurations are subject to the same limitation.

The only way to avoid excessive noise bandwidth is to restrict the frequency range of the op amp. By doing so, the control of the noise response switches from the  $1/\beta$  curve to the amplifier roll-off. Where the op amp has provision for external phase compensation, this control is a simple matter and permits you to remove bandwidth from signal and noise alike. However, because most op amps lack an external-phase-compensation facility, passive filtering within the feedback loop offers a broader solution (Ref 3). Such filtering introduces a capacitive shunt to ground following the amplifier but within the feedback loop.

You can also demonstrate the extended noise bandwidth of an integrating converter using a feedback plot but, more importantly, the curves illustrate the dynamic-range limit for integrator-based instrumentation. In Fig 4, the integrator  $1/\beta$  curve also levels off at the unity-gain line for continued noise gain out to where the op amp rolls off. Be aware that this action has far less noise significance for the integrator because of its increasing gain at lower frequencies. Integrators designed for operation to 1 kHz or even higher are generally unaffected by the added noise bandwidth.

Nevertheless, the feedback plot for the integrator demonstrates a unique bandwidth limitation involving two critical intercepts. Not only does the  $1/\beta$  curve intercept the gain-magnitude curve at the high-frequency extreme, but it does so at the low-frequency end as well. Each intercept indicates a lack of amplifier gain for support of the feedback and a departure from the ideal response. At the high end, the  $1/\beta$  curve and noise-gain level off, leaving  $A_{CL}$  to continue as long as the loop gain lasts. Next,  $1/\beta$  intercepts the gain-magnitude curve at  $f_c$  where the noise gain rolls off.

This intercept is a high-frequency 3-dB point for the integrator response, which then usually rolls up rather than down. Upward response in this region is due to signal feedthrough caused by the feedback elements

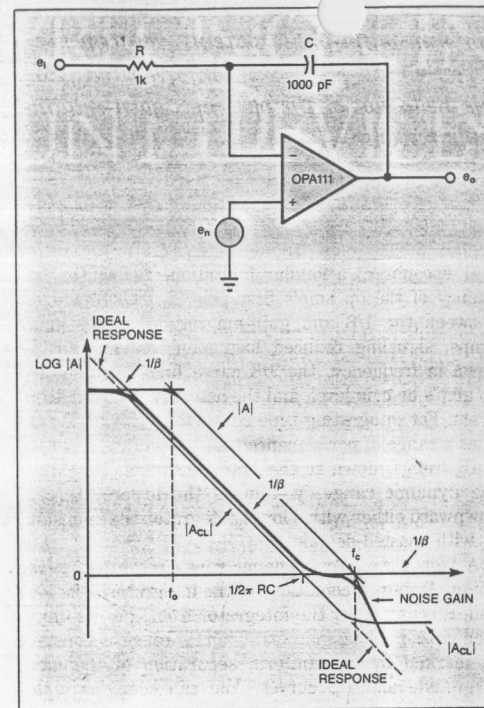


Fig 4—Defining the dynamic range for integrating data converters, the integrator  $1/\beta$  curve displays upper and lower intercepts with the gain-magnitude response.

in the absence of loop control. At the lower frequencies, the increasing gain demand encounters the dc gain limit of the op amp. This intercept marks the second 3-dB point for the integrator response, which sets the range for accurate performance. Both intercepts have a 20-dB/decade rate-of-closure, indicating stable operation.

#### Consider the gain error

Between the two integrator-response limits is the usable dynamic range for dual-slope A/D and V/F converters. The gain error limits this dynamic range; the plots are a graphic representation of this error. The gain error is inversely related either to a circuit's loop gain or the difference between the amplifier's open-loop gain and the feedback demand of  $1/\beta$ . On the response plots, the gain error is the vertical distance between the two curves. For the Fig 4 integrator, this separation decreases following  $1/\beta$ 's encounter with the unity-gain axis. From there, the separation finally reduces to zero at  $f_c$ . The gain error then becomes the distance between the dashed continuation of the ideal integrator response and the actual  $A_{CL}$  response. Graphically, this distance is the source of the large-signal limitation for integrating converters where higher signals correspond to the upper frequencies.

At the other end of the converter range, lower-level





age gain, you cannot draw the signal-gain curve on the gain-magnitude response to estimate bandwidth. When you inspect the circuit to ascertain its bandwidth limitation, you'll see that the only inherent break frequency is that of the feedback resistance and the capacitance of the input circuit. By plotting the  $1/\beta$  curve, however, you can see that the loop gain remains to support the ideal feedback condition far beyond the  $f_i$  break frequency.

Initially, the  $1/\beta$  curve is flat at unity because of the direct output-to-input connection of  $R_f$ . When the feedback is later shunted by  $C_D$  and  $C_{ia}$ ,  $1/\beta$  rises at a 20-dB/decade rate. The transition between these regions occurs at

$$f_i = 1/2\pi R_f(C_D + C_{ia}),$$

where  $C_{ia} = C_{id} + C_{icm}$ .

The intercept with the gain-magnitude curve marks the end of the response rise for the noise gain. This curve has a -20-dB/decade slope so, if left uncompensated, the rate-of-closure at the intercept will be 40 dB/decade. Thus, the plot indicates two poles at that intercept frequency,  $f_p$ . This intercept is the point at which there is no longer sufficient amplifier gain for the feedback-factor demand, and it indicates response roll-off independent of the op-amp function. Any amplifier function would then roll off with a slope equal to the rate-of-closure.

#### Stability depends on phase compensation

Because the rate-of-closure is 40 dB/decade, you should examine phase shift at the intercept to determine the phase compensation necessary for stability. When the various break frequencies are well removed from the intercept, the rate-of-closure accurately reflects 180° of phase shift for the uncompensated loop. To avoid oscillation and to achieve good damping characteristics, you must reduce this phase shift by at least 45° through roll-off of the  $1/\beta$  curve.

According to the Bode phase approximation, this phase shift is the amount of phase introduced at a break frequency. Choosing  $C_f$  to break with  $R_f$  at the intercept frequency,  $f_p$ , yields 45° of phase margin. Accompanying this phase condition is a 3-dB peak in the signal response, which for a 2-pole response pushes the -3-dB bandwidth out to  $1.4f_p$ . For the OPA111 and the feedback elements shown, the 3-dB response extends to 48 kHz. (You can extend this analysis to lower capacitance levels, and the common solution

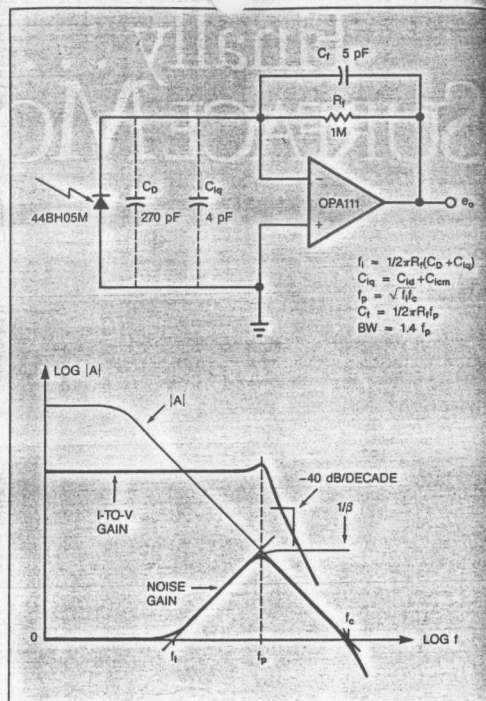


Fig 6—A photodiode amplifier's current-to-voltage function serves to obscure its bandwidth and stability, but you can rely on feedback-loop conditions to define its performance.


mentioned above will still suffice—even for the high-feedback-resistance case of Fig 5.)

As long as  $C_f$  breaks with  $R_f$  at the frequency of the intercept, the  $1/\beta$  rise contributes no more than 45° of phase shift. In the range where the op-amp phase shift is 90°, this rise leaves a stable 45° phase margin. Nevertheless, as the op amp approaches its crossover frequency,  $f_c$ , its contribution to phase shift moves toward 135°. The rule of thumb for selecting  $C_f$  remains valid, however, because any intercept near  $f_c$  must be a result of a  $1/\beta$  rise of short duration. The added phase shift of the amplifier, accompanied by a necessary decrease in feedback phase shift at the intercept, results in a net zero effect. By simple sketching of the phase approximations for the  $1/\beta$  and gain-magnitude curves, you can show this transition.

#### Simple, yet elegant

To select the compensation capacitance, it is desirable to reduce the graphical analysis to an equation. Luckily, the response plots provide an elegantly simple solution. Straight-line extensions of the  $1/\beta$  and gain-magnitude curves form a triangle with the horizontal axis. These extensions have equal but opposite slopes, which form an isosceles triangle. The peak of the triangle, located over the center of its base, lies at the average of the base end points. Mathematically, this

# NEVER HEARD OF THEMIS?

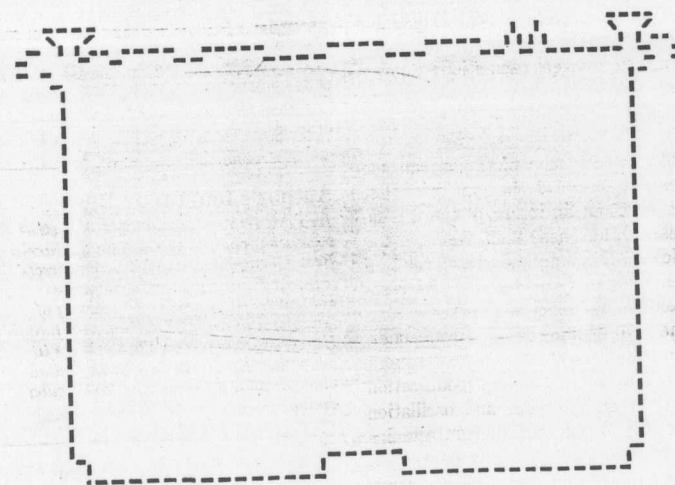

average point is equal to

$$\text{Log } f_p = (\text{Log } f_i + \text{Log } f_c)/2.$$

Given the expressed logarithmic nature of the frequency axis, you can reduce this relationship to the simple geometric mean of the two characteristic frequencies:

$$f_p = \sqrt{f_i \times f_c},$$

where  $f_i = 1/2\pi R_f(C_D + C_{id} + C_{icm})$ , and  $f_c$  equals the unity-gain bandwidth of the op amp.

For a third input-circuit effect, the  $1/\beta$  curve demonstrates stable conditions where typical gain and phase plots would point to oscillation. In addition to input capacitance, op amps have input inductance; this combination produces a high-frequency resonance. The inductance is small but inescapable, being associated with internal input wires and being compounded by external wiring.

When it comes to high frequency . . .

For very high-frequency amplifiers, like the OPA620 video amplifier of Fig 7, sufficient amplifier gain exists at the resonant frequency to give the appearance of zero gain margin. A comparison of the output signal ( $e_o$ ) with that at the summing junction ( $e_i$ ) produces the plot's gain and phase responses. Following unity crossover, the gain curve rises again above the unity axis; this rise generally guarantees oscillation for lower gain levels. Adding to stability concerns is the phase plot, which swings wildly through  $180^\circ$  during the gain peak.

By adding the  $1/\beta$  curve to the plot, you can see that this curve does not intersect the gain peak but merely rides over it. Without an intercept there is no oscillation, regardless of the phase shift, because the loop gain is insufficient. Loop-gain demand rises in synchronization with the gain peak because the resonant circuit also alters the feedback network.

In many cases, the gain peaking results from conditions in the amplifier output rather than from the input circuit. In such a case, no corresponding modification of feedback occurs, and an intercept and oscillation result. However, for Fig 7, the gain margin remains high, as you can see by the separation between the  $1/\beta$  curve and the gain response when the phase reaches  $180^\circ$ . This separation remains large throughout the region of higher phase shift, indicating good relative stability.

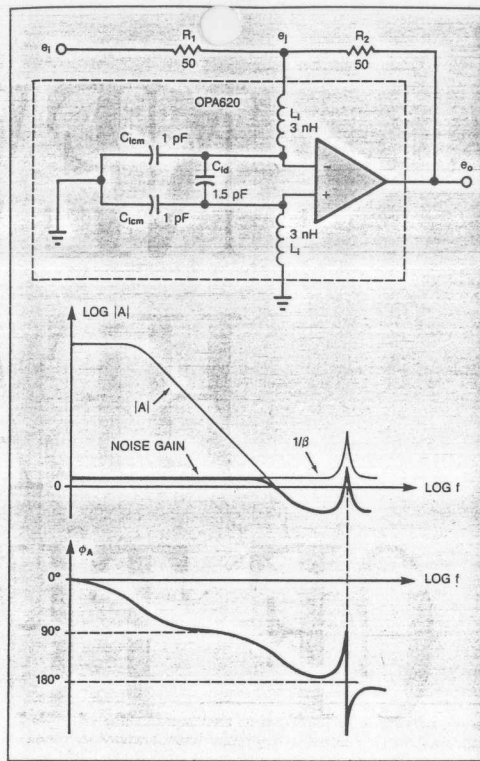


Fig 7—Although amplifier gain and phase plots suggest instability, the  $1/\beta$  curve shows stable conditions for a circuit with input-lead inductance.

## References

1. Tobey, G, J Graeme, and L Huelsman, *Operational Amplifiers: Design and Applications*, McGraw-Hill, New York, NY, 1971.
2. Bower, J, and P Schultheiss, *Introduction to the Design of Servomechanisms*, Wiley, New York, NY, 1961.
3. Stitt, M, and R Burt, "Möglichkeiten zur Rauschunterdrückung," *Elektronik*, December, 1987, pg 112.

## Author's biography

Jerald G Graeme is manager of instrumentation-components design at Burr-Brown Corp (Tucson, AZ), and directs a linear-IC development group. He holds a BSEE from the University of Arizona and an MSEE from Stanford University. Jerry has eight patents to his credit. His leisure pursuits include photography, woodworking, and scuba diving.



Article Interest Quotient (Circle One)  
High 488 Medium 489 Low 490

EDN

# KNOW-HOW, EFFICIENCY AND RELIABILITY DON'T ALWAYS MAKE A LOT OF NOISE...

## THEMIS : FIVE YEARS' EXPERIENCE IN VME-CARDS

Belonging to a large French industrial group, we have taken part in the elaboration of the VME-card. We have thus acquired a unique experience in industrial cards.


## THEMIS : SOLUTIONS THAT WORK, SOLUTIONS THAT ARE ALWAYS SUITED

Based on 32 bits CPU, we have developed a complete range of intelligent couplers specifically aimed at your industrial applications: robotics, graphics, communications, signal processing, etc.

Mastering UNIX, OS/9, and pSOS have made us the unquestioned specialists in real-time (UNIX/pSOS link).
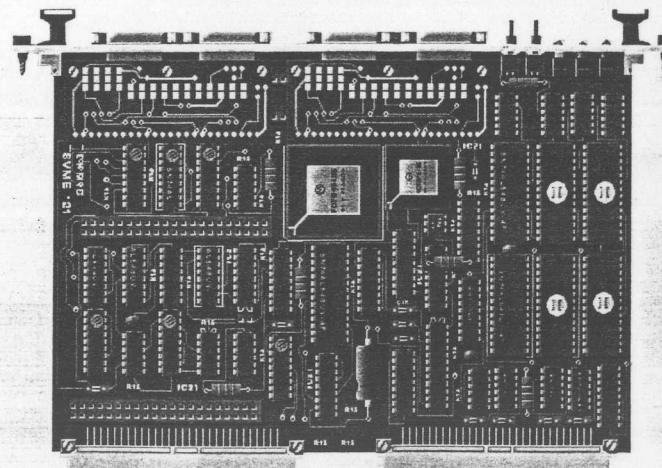
## THEMIS : INDUSTRY'S SPECIAL PARTNER

From definition all the way up to on-site integration, our teams of engineers will always be there to discuss with you to make sure that the achievements and reliability of your applications are optimised.



AUSTRIA: REKURSCH ELEKTRONIK TEL: (43) 222 25 36 26/0 - DENMARK: SCANSUPPLY A/S TEL: (45) 183 50 90 - FINLAND: TAHINIK OY TEL: (35) 80 566 32 33 - FRANCE: TEKELEC TEL: (33.1) 45 34 75 35 - CODICOM (SILEC) TEL: (33.1) 43 75 95 92 - GERMANY: TEKELEC AIRTRONIC GMBH TEL: (49) 89 51 640 - ALLMOS ELECTRONIC GMBH TEL: (49) 857 00 00

ITALY: LASI ELETTRONICA S.p.A. TEL: (39) 2 24 40 012/210 - TEKELEC AIRTRONIC TEL: (39) 2 73 80 642 - NORMAY: TAHONIC A.S. TEL: (47) 2 16 18 10 - SWEDEN: TH'S ELEKTRONIK AB TEL: (46) 8 36 29 70 - SWITZERLAND: MODULATOR S.A. TEL: (41) 59 22 22 - U.K.: KORAL MICROSYSTEMS LIMITED TEL: (44) 954 50 826 - TEKELEC COMMUNICATION LIMITED TEL: (44) 734 771 020

THEMIS 29, AVENUE DE LA BALTIQUE - ZA DE COURTABOEUF - 91953 LES ULIS CEDEX FRANCE  
TEL: (33.1) 69 86 15 25 - TELEX: 603 347 - FAX: (33.1) 64 46 45 50



# WANT TO TALK SCSI? CALL CIPRICO AT 1-800-SCSI-NOW.

Why talk SCSI with Ciprico? To start with, we're the only vendor with a complete line of high-performance SCSI host bus adapters for Multibus\* I, VMEbus, and Multibus II. Each board was designed to optimize performance with its system bus. And consider our experience. Ciprico has over 50,000 boards installed worldwide. Our design expertise provides you with the highest possible performance at the lowest possible price.

But that's not all. Ciprico has *responsibility*. We have the largest staff of customer support engineers in the industry to help you resolve any integration problems. Plus software drivers for all major operating systems.

Our SCSI adapters are all based on an 80186 microprocessor, providing a command queuing, pass-through SCSI command software interface. Each board supports SCSI disconnect/reconnect and asynchronous and synchronous transfer rates of 2MB/s and 5MB/s respectively. And a floppy port is optional for cost effective system design.

So if you're currently designing a system based on Multibus I, VMEbus, or Multibus II, give us a call to talk SCSI.

RIMFIRE 3510  
SCSI Adapter for  
VMEbus

RIMFIRE 2500  
SCSI Adapter for  
Multibus\* II

RIMFIRE 1500  
SCSI Adapter for  
Multibus\* I

**CIPRICO**  
2955 Xenium Lane  
Plymouth, MN 55441  
CIPRICO LISTENS. AND RESPONDS.

Multibus is a registered trademark of Intel Corporation.

CIRCLE NO 69

EDN February 2, 1989



op-amp feedback  
circuits  
Part 2


## Bode plots enhance feedback analysis of operational amplifiers

*Bode plots graphically represent an op amp's gain, phase-margin, and noise characteristics. Part 1 of this series (Ref1) covered the feedback analysis of single-stage operational amplifiers; the conclusion examines the feedback behavior of composite op-amp circuits.*

Jerald G Graeme, Burr-Brown Corp

Whereas the normal op-amp feedback loop involves only one amplifier, designers oftentimes need to extend the feedback loop to work with composite circuits that use two or more op amps for increased gain. By adhering to conventional feedback principles, you can implement phase compensation for the extended loop and rely on a Bode plot to provide a visual representation of the increased gain and the opportunity for extended bandwidth.

For instance, with two op amps in the same loop as in Fig 1, you can achieve increased gain without incurring any added offset and noise error. The input-error effects of the second amplifier are divided by the open-loop gain of the first amplifier. The net open-loop gain of this composite circuit becomes the product of the individual op-amp gains and greatly reduces the overall gain error and nonlinearity.

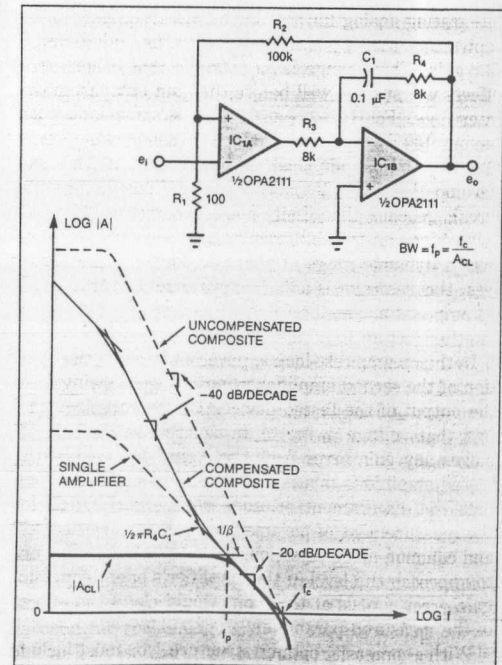

**Fig 1—To utilize the boosted gain of the composite amplifier, traditional phase-compensation techniques tailor the gain-magnitude slope to obtain a stable region with a  $1/\beta$  intercept.**

*With a composite amplifier, a designer can selectively optimize the performance characteristics of both the individual op amps and the overall circuit.*

In Fig 1, the two op amps are those of the dual OPA2111, which imposes only a modest cost increase over a single device. You could, of course, select individual op amps to provide specific performance characteristics. In the latter case, you might select the input amplifier for good dc and noise performance and the output amplifier for its load-driving and slewing performance. For example, the output amplifier could handle the load current and the resulting power dissipation, thus producing no thermal feedback to the input of the composite circuit. Moreover, it could also fulfill the high-slew-rate demands of the application. The input amplifier in this case would only swing through small signals.

#### Extending the dynamic range is feasible

An integrator and a common op-amp test loop can demonstrate the benefits of using a composite amplifier. By extending the composite open-loop gain to higher levels, you can expand the dynamic range for integrating analog functions. The low-frequency intercept moves back by a factor equal to the added amplifier gain. This change is so extreme that other error effects will surface well before the gain error from the intercepts. For two op amps in the same loop each having 100-dB open-loop gain, the composite gain is -200 dB. At this gain level, an input error of 1 nV will develop the full 10V output swing. Long before the circuit reaches that limit, noise becomes a prime ac constraint and typically restrains lower-level accuracy over a dynamic range of about 3,000,000:1. Nevertheless, this restraint is a 30:1 improvement over a single op amp and moves the focus of measurement accuracy to other factors.

In the op-amp test-loop application (Ref 2), the addition of the second amplifier removes signal swing from the output of the tested device. The extra gain transfers that voltage swing to an isolated output and removes any gain error from the signal detected at the tested amplifier's inputs. This gain-error removal permits the discernment of other input-error signals for the measurement of parameters such as power-supply and common-mode rejection. If these parameters were to approach the level of the amplifier's open-loop gain, gain-error signals at the input would cloud the effects of the measured parameter.

With a composite op-amp structure, you must include the roll-off characteristics of both amplifiers in your ac analysis and have some means of providing phase compensation for the loop. Two op amps in a common

loop invite oscillation; the individual amplifier poles combine for a composite 2-pole roll-off. As shown in Fig 1, the logarithmic scale makes the initial composite-response curve the linear sum of the two individual responses. The upper, dashed response curve, which has a -40-dB/decade slope, shows this result.

Two methods are available for compensating the composite loop. One modifies the gain-magnitude response and the other alters the 1/β curve. The more usual of the two approaches is to reduce the slope of the gain-magnitude curve in the vicinity of the intercept—as Fig 1 does. After forcing the compensated response to roll off earlier, the gain-magnitude curve returns with a more gentle slope to the boundary of the uncompensated response. This action serves the general-purpose requirements of voltage-gain applications and produces a stable range that you can place almost anywhere in the total composite-gain range.

Fig 1 achieves this compensation by creating a modified integrator response for IC<sub>1B</sub>. Because this integrator is an inverting circuit, the inputs of IC<sub>1A</sub> are reversed to retain only one phase inversion in the loop. Capacitor C<sub>1</sub> blocks the local dc feedback, and the overall gain is still the product of the two open-loop gains. The integrator response that R<sub>3</sub> and C<sub>1</sub> established for IC<sub>1B</sub> rolls off this composite gain. Next, the first open-loop pole of IC<sub>1A</sub> returns the compensated response slope to -40 dB/decade. At a higher frequency, a response zero provides the region of reduced slope thanks to the inclusion of R<sub>4</sub>. Above the break frequency of R<sub>4</sub> and C<sub>1</sub>, R<sub>4</sub> transforms the response of IC<sub>1B</sub> from an integrator to an inverting amplifier with a gain of -R<sub>4</sub>/R<sub>3</sub>.

Where this gain is unity, the compensated response drops to and follows the open-loop response of IC<sub>1A</sub> as shown. For gain levels other than unity, you have different options, which you can explore by using other response plots and defining the particular stable conditions you have in mind. Having control of this gain becomes particularly useful as the 1/β intercept approaches the uncompensated unity-gain crossover point. In this region, the second poles of the two op amps increase the phase shift. In such cases, you have to make the magnitude of the internal R<sub>4</sub>/R<sub>3</sub> gain less than unity to force the compensated response to cross over earlier. Generally, when you have two op amps of the same type, making R<sub>4</sub> = R<sub>3</sub>/3 will yield a unity-gain stable composite amplifier.

The net phase correction that you can achieve with this technique depends on the frequency-response

range for which you maintain the -20-dB/decade slope. This span begins with the R<sub>4</sub>C<sub>1</sub> break frequency and ends with the intercept of the composite open-loop response. After this intercept, the lack of open-loop gain returns the response to that of the uncompensated composite amplifier. To ensure a phase margin of 45° or more, you can use the guidance that the Bode phase approximation provides; the plot shows that this reduced slope region must last for three decades of frequency and must intercept the 1/β curve after running for at least a decade.

#### Extending the bandwidth may be desirable

Although most engineers are familiar with this type of phase compensation, it is too restrictive of bandwidth at higher gains. For applications requiring higher gains, you can greatly extend the bandwidth and reduce the settling time by 40:1 by using a different phase-compensation technique. The general-purpose

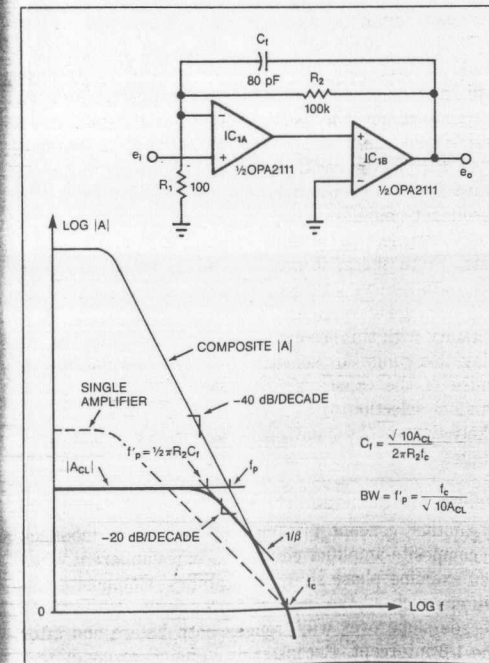


Fig 2—For greater bandwidth in high-gain circuits, you can provide phase compensation for the 1/β response to retain a smooth open-loop response for fast settling.

R<sub>4</sub> = R<sub>3</sub> case of Fig 1 sets a constant closed-loop gain-bandwidth product. Looking at the curves, you can see that the closed-loop bandwidth is the same as that for IC<sub>1A</sub> itself when BW = f<sub>p</sub> = f<sub>c</sub>/A<sub>CL</sub>. Even so, the large separation between the compensated and uncompensated responses shows a significant sacrifice in bandwidth—expressly for the accommodation of phase compensation. Uncompensated, the gain-magnitude response has a gain-bandwidth product that increases with closed-loop gain and that provides a potential bandwidth of f<sub>p</sub> = f<sub>c</sub>/√A<sub>CL</sub>. Comparing the last two expressions shows that the potential for bandwidth improvement equals √A<sub>CL</sub>, which is significant at higher gains.

#### Another way is to compensate the 1/β curve

You can take advantage of quite a bit of this bandwidth-improvement opportunity by compensating the 1/β curve instead of the gain-magnitude response curve. By referring back to the rate-of-closure stability criteria discussed in Part 1 (Ref 1), you would see that both curves contribute to the rate-of-closure parameter even though the gain-magnitude curve is generally the focus of phase-compensation efforts. To satisfy the rate-of-closure criteria, all that is necessary is to control the difference between the slopes, regardless of the slopes of the individual curves. So, instead of reducing the gain-magnitude slope, increase the 1/β slope (Fig 2). A simple capacitive bypass of feedback resistor R<sub>2</sub> accomplishes this slope increase for a final 20-dB/decade rate-of-closure. An integrator configuration, on the other hand, with its special characteristics, inherently produces the -20-dB/decade slope for 1/β and achieves optimum bandwidth and dynamic range.

From a phase-shift perspective, this alternative approach to compensation adds phase shift to 1/β instead of subtracting it from the gain-magnitude response. It pushes the net phase shift beyond 180° toward 270°, rather than pulling it back toward 90°. In either case, the resulting phase margin approaches 90°, but the Fig 2 method is simpler and achieves greater bandwidth. The pole created with C<sub>1</sub> sets the bandwidth instead of the 1/β intercept.

Two factors distinguish this feedback-factor compensation technique for higher gains. Greater bandwidth is open for reclaiming, and the associated 1/β curves are well above the unity-gain axis. From higher levels, the 1/β roll-off is developed well before its intercept with the gain-magnitude curve. Starting this roll-off a decade ahead of the final intercept produces a 45° phase



Two methods are available for compensating the composite feedback loop. One modifies the gain-magnitude response, the other alters the  $1/\beta$  curve.

adjustment for a like amount of phase margin. The slopes of the two curves show that, in order to accomplish this phase adjustment,  $C_f$  must break with  $R_2$  one-half decade below the initial intercept frequency,  $f_p$ . Then, the 2:1 difference in slopes will place the new intercept one-half decade above  $f_p$  for the required full decade of the  $1/\beta$  roll-off.

#### Time to brush up on equations

Again, the design equations for the required value of  $C_f$  and the resulting bandwidth are obvious from the logarithmic nature of the frequency axis. Setting  $f_p'$  at one-half decade below  $f_p$  implies that

$$\log f_p' = (\log f_p + \log f_p/10)/2,$$

for which  $f_p' = f_p/\sqrt{10}$ . From before, you'll remember that  $f_p = f_c/\sqrt{A_{CL}}$  describes the uncompensated curve's bandwidth. The compensated bandwidth is

$$BW = f_p' = f_c/\sqrt{(10A_{CL})}.$$

Here,  $f_c$  is the unity-gain crossover frequency of the composite gain-magnitude response. As becomes obvious when you examine this expression, the improved bandwidth falls short of the total potential by  $\sqrt{10}$ . However, it is better than the Fig 1 result by  $\sqrt{(A_{CL}/10)}$ , or a factor of 10, for a gain of 1000. Setting  $C_f$  to break with  $R_2$  at  $f_p'$  defines the value of this capacitor as

$$C_f = \sqrt{(10A_{CL})}/2\pi R_2 f_c.$$

For the op amps of the dual OPA2111 shown, the gain-of-1000 bandwidth becomes 20 kHz as compared with the 2 kHz you'd realize if you used just one of the op amps.

#### Improving the settling time

Settling time also improves when you choose the composite amplifier's  $1/\beta$  curve for phase compensation. The improvement is a result of both the increased bandwidth and the retained constant gain-magnitude slope. For a single amplifier of the OPA2111 type, for a gain of 1000, the settling time would be 700  $\mu$ sec to 0.01%. Because the Fig 2 amplifier has 10 times the bandwidth of a single amplifier, the settling time drops by the same factor to 70  $\mu$ sec. This improvement would not be possible without the smooth and continuous

slope of the compensated-amplifier response. A response having an intermediate pole and zero such as Fig 1 does has low-frequency response terms that are slow to settle following a transient. Known as an integrating frequency doublet, this pole/zero combination is notorious for its poor settling time (Ref 3). By providing phase compensation for the  $1/\beta$  curve, you ensure that the smooth gain-magnitude curve is left undisturbed, therefore achieving the optimum settling time.

At lower gains, the benefit of the  $1/\beta$  compensation technique diminishes as does its control of phase. Because lower gains have  $1/\beta$  curves closer to the unity-gain axis, they have less room for  $1/\beta$  roll-off. To produce an intercept with the gain-magnitude curve after a decade of  $1/\beta$  roll-off requires a minimum closed-loop gain of 10. Op-amp phase shifts impose further limits by growing from 90° to 135° as they approach the unity-gain crossover frequency. In the practical case, this phase-compensation method needs gains of 30 or more for good stability.

This type of phase compensation does have an unusual aspect: Too great a compensating capacitance will have a surprising effect. Whereas increasing such capacitance normally yields more damping and a more stable response, making  $C_f$  too large will cause instability. As  $C_f$  increases, the resulting intercept moves toward  $f_c$  and encounters the added phase shift of the secondary-amplifier poles. Even greater values of  $C_f$  will drop the  $1/\beta$  curve to its limit at the unity-gain axis. From there, it proceeds along the axis to the magnitude-curve intercept that guarantees oscillation. Only a range of compensation-capacitor values provides stability with this second approach; the  $1/\beta$  curves display this range for sensitivity-analysis purposes. Because of the capacitor's window of stable values, a random selection of  $C_f$  followed by a stability test is likely to miss the bandwidth opportunity of this technique.

#### Phase shift and stability come next

Another concept fundamental to op-amp feedback in composite-amplifier circuits becomes apparent when you examine phase shift and stability. Composite amplifiers such as the one in Fig 3 produce a -40-dB/decade slope over wide ranges both before and after the  $1/\beta$  intercept. Because this slope corresponds to a 180° phase shift, frequent concern over stability conditions arises at points other than that of the critical intercept. Beyond the  $1/\beta$  intercept, the loop gain is

less than 1 and therefore it is easy to see that the circuit cannot sustain oscillation. Yet, prior to the intercept, the gain of the feedback loop is very high and would seem capable of causing the circuit to oscillate.

In reality, the high loop gain is a protection against, rather than a promoter of, oscillation. Sustained oscillation depends on the op amp's gain-error signal. In Fig 3, the gain error,  $e_o/A$ , appears between the op-amp inputs and receives amplification from the closed-loop gain,  $A_{CL}$ . Here,  $A_{CL}$  is that of the noninverting configuration, the noise gain that reacts with any input-referred error signal. To sustain oscillation, the amplified error signal must independently deliver the output signal. This action requires that  $(-e_o/A)A_{CL} = e_o$ . Note that  $e_o$  appears on both sides of this equation; it should therefore be obvious that any solution must conform to very specific constraints. This equation expresses both polarity and magnitude constraints; the composite amplifier's 180° phase shift satisfies the sign change.

For the magnitude constraint, two possible solutions exist. The first is  $e_o = 0$ , which is the stable state for

the composite amplifier in the questioned region. There, the loop gain makes the signal  $e_o/A$  too small to independently support an output signal. In the plots of Fig 3,  $e_o/A$  starts at a very low level due to the high loop gain at low frequencies. As you move up in frequency, the gain-error signal rises while the amplifier-response slope signals its polarity inversion through the 180° phase shift. This inversion increases the output signal but cannot sustain it until the gain-error signal reaches a sufficient level. This critical level is a prerequisite for oscillation.

This level applies to the second solution for the magnitude constraint. At this level,  $A/A_{CL}$  has unity magnitude and maintains the balance for the previous feedback equation's magnitude requirement. Unity loop gain occurs at the  $1/\beta$  intercept where the open-loop and noise-gain curves meet. Without phase-compensation intervention, this intercept satisfies both the phase and magnitude requirements for oscillation. Beyond this point,  $e_o$  and  $A$  fall off together, leaving the  $e_o/A$  signal constant and unable to support oscillation with the reduced gain. At the point where the magnitude of the gain error and the feedback phase shift must both reach specific levels to support oscillation, the intercept becomes critical. Before or after the intercept, the loop phase shift can be at any level and the gain-error magnitude will not be sufficient to cause instability.

Unfortunately, despite the composite amplifier's very specific requirements for oscillation, the greatly varied applications of op amps make this critical condition all too easy to encounter. To contend with this problem, you can rely on the  $1/\beta$  curve to present a visual prediction of the problem and provide insight into a solution.

#### Variable feedback helps

Some applications demand that you include a second active element in the feedback loop to produce a varying feedback factor. In these applications, both the magnitude and the frequency characteristics of  $1/\beta$  become variables. Fortunately, the gain- and feedback-response curves offer a means of quickly evaluating the range of conditions resulting from the changing feedback.

The most common way to provide magnitude variation in the feedback factor is to use a low-cost analog divider realization. Placing a multiplier in the feedback loop of an op amp (Ref 4) makes feedback a function of a second signal and therefore produces divider opera-

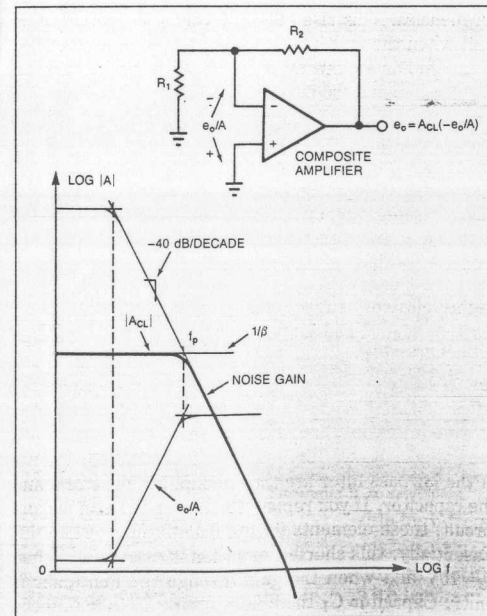


Fig 3—A phase shift of 180° causes oscillation only where the gain-error,  $e_o/A$ , is capable of independently supporting the output signal.

Various phase-compensation techniques are available to tailor the circuit's bandwidth and settling time.

tion. With signal-dependent feedback, the bandwidth and stability conditions also become variables.

Fig 4 shows the divider connection and demonstrates the effect of voltage-controlled feedback on  $1/\beta$ . The amplifier's feedback inverts the function of the multiplier by placing the feedback signal under the control of the  $e_2$  signal. Then, the multiplier's transfer function of XY/10 delivers  $e_0(e_2/10)$  to  $R_2$ . This action scales the feedback signal by comparing  $e_2$  to a 10V reference level to obtain

$$\beta = (e_2/10)R_1/(R_1 + R_2).$$

With the feedback factor under control of this signal, the  $1/\beta$  curve moves across the full range of the gain-magnitude response. As  $e_2$  nears zero, the  $1/\beta$  curve approaches infinity, leaving the op amp essentially in an open-loop configuration. At the other extreme, a full-scale 10V value for  $e_2$  delivers a feedback signal to  $R_2$  that equals  $e_0$  almost as if the multiplier were not present. Then, the net response is that of a simple

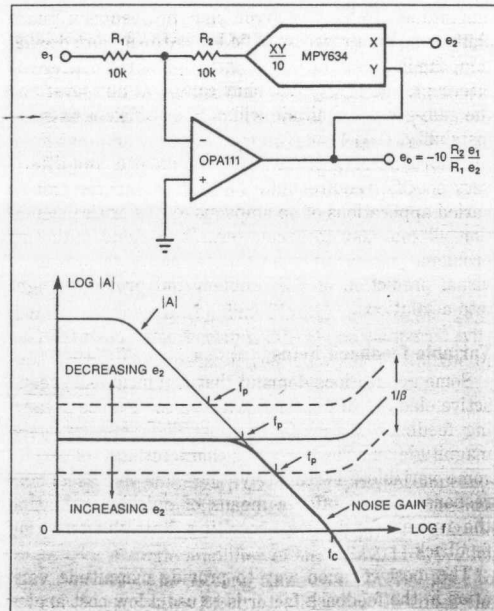


Fig 4—For this common analog divider, a variable feedback magnitude allows a range of conditions that define bandwidth and stability.

inverting amplifier with a feedback factor of  $R_1/(R_1 + R_2)$  and an inverting gain of  $-R_2/R_1$ .

#### From one extreme to the other


Between the extremes, the variation of  $e_2$  moves the  $1/\beta$  curve from as low as the unity-gain axis to above the upper reaches of the amplifier's gain-magnitude curve. This variation moves the critical intercept and requires attention to the rate-of-closure over the entire span of the gain-magnitude response. If no significant multiplier phase shift exists, the feedback will always resemble that of an inverting amplifier for a zero  $1/\beta$  slope, and you can ensure stability by just using a unity-gain-stable op amp. You can then read the range of bandwidth for the divider operation directly from the moving  $1/\beta$  intercept. For a given  $e_2$  range, the intercept moves linearly with the signal, defining the corresponding bandwidth range.

The multiplier also introduces phase shift that alters the net phase shift around the feedback loop. Poles in the response of the multiplier circuit are zeros in the inverse  $1/\beta$  function, causing the curve to rise at high frequencies. This rise moves toward the critical intercept when the multiplier control voltage,  $e_2$ , increases. This rise has an impact on the rate-of-closure, and the op amp must introduce a dominant pole to maintain stability. For the components shown, the OPA111 dominates the circuit roll-off because of its 2-MHz unity-gain crossover frequency. This frequency is well below the 10-MHz bandwidth of the MPY634 multiplier, placing the op amp in control. Other options that use a separate feedback path to restrict the op-amp bandwidth are also available (Ref 5).
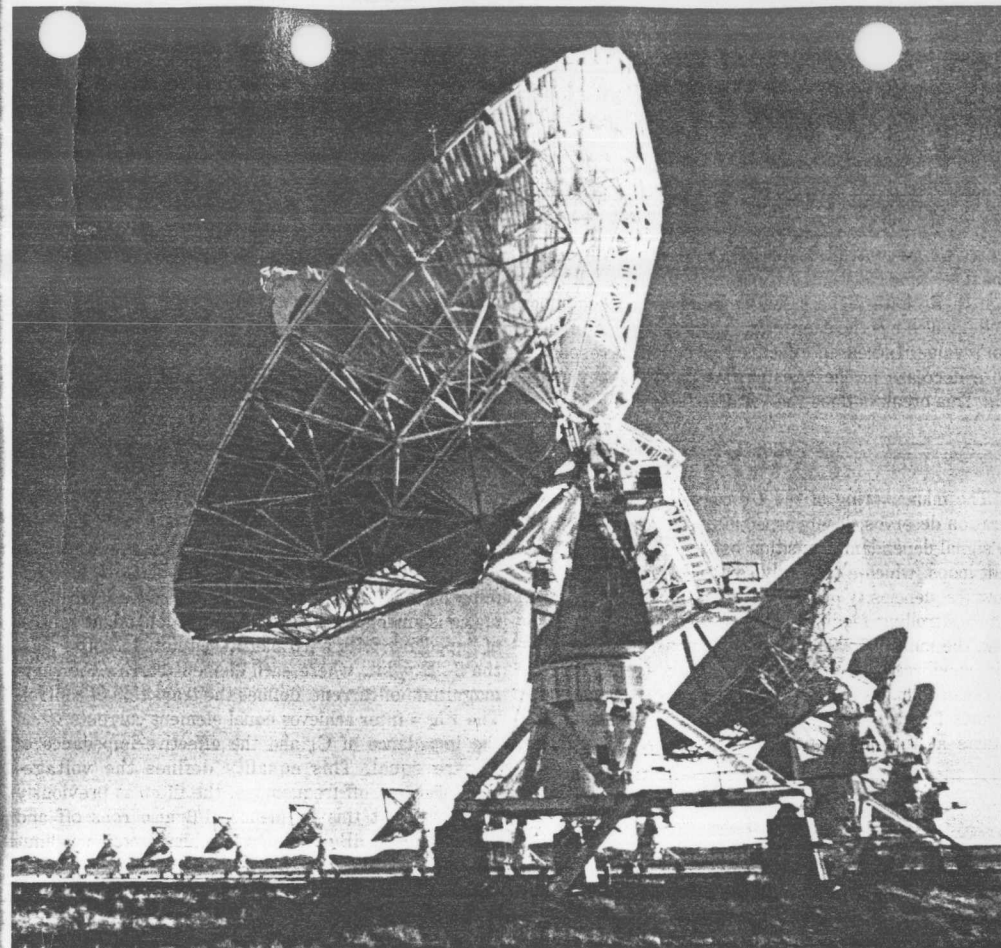
#### Signal control of frequency characteristics

Other ways of providing variable feedback are also available. For example, you can have the signal control the frequency—rather than the magnitude—characteristics of the feedback. The result is a variable slope at the intercept, as is the case with the voltage-controlled lowpass filter in Fig 5. The basic elements of the lowpass filter are the op amp, the resistors, and the capacitor. If you replace the multiplier with a short circuit, these elements form a fixed-frequency roll-off. Essentially, this shorted condition is established when  $e_2 = 10V$  and when the gain through the multiplier is unity. Capacitor  $C_1$  then breaks with  $R_2$  to define the filter roll-off just as if the resistor and capacitor were directly in parallel.

For levels of  $e_2$  below full scale, the multiplier serves



## NOTHING TAKES EVERYTHING YOU CAN DISH OUT LIKE MICRO/Q® 2000 CAPACITORS.

For applications in severe conditions, nothing can take whatever the environment dishes out like Rogers new Micro/Q 2000 Flat Ceramic Decoupling Capacitor.

Nothing takes the heat or cold or humidity like Micro/Q 2000 with its unique molded construction and X7R dielectric.

Nothing takes up less space because only the Micro/Q 2000 fits under DIPs to save valuable board space. Retrofit to sim-

ply design. Supplied in anti-static tubes.

Nothing is as effective at reducing voltage noise spikes. Only Micro/Q 2000 provides the low-inductance and impedance levels necessary to reliable high-frequency decoupling.

The new Micro/Q 2000 from Rogers. Nothing you can design with works or fits like it—even in the harshest environments.

Test results for MIL-C-39014D and MIL-STD-202F are available. Call or write a Rogers Micro/Q application engineer today for test results, free samples and technical information.

Another MEKTRON® interconnection component.

**ROGERS**

Rogers Corporation  
Circuit Components Division  
2400 South Roosevelt St.  
Tempe, AZ 85282  
Tel: (602) 967-0624  
Fax: (602) 967-9385

OUTSIDE THE U.S. CONTACT: Europe: Mektron NV, Ghent, Belgium Japan: Rogers Inoue Corp., Nagoya  
Brazil: Rogers Coselbra, Sao Paulo Singapore, Hong Kong, Taiwan: Dynamar



When you use a second active element in the feedback loop, both the magnitude and frequency characteristics of  $1/\beta$  become variables.

as a voltage-controlled attenuator to effectively alter the filter time constant. Attenuating the feedback voltage to  $R_2$  lowers the signal current to the summing node, which has the same effect as increasing the resistor's value. Increased effective resistance corresponds to a decrease in the resistor's break frequency with  $C_1$ . This break defines the variable filter roll-off when

$$f_p = e_2 / 20\pi R_2 C_1.$$

The maneuvering of the  $1/\beta$  curve through this operation deserves closer inspection. The circuit exhibits a signal-dependent transition between the two different loops, which alternately controls the feedback. At low frequencies,  $C_1$  is effectively an open circuit, and the controlling feedback path is through the op amp and the multiplier. This composite structure has resistive feedback that defines a signal gain of  $-R_2/R_1$  and a noise gain of  $(R_1 + R_2)/R_1$ . The latter relationship equals  $1/\beta$  at low frequencies and the curve of interest starts at this level with a zero slope. At the high-

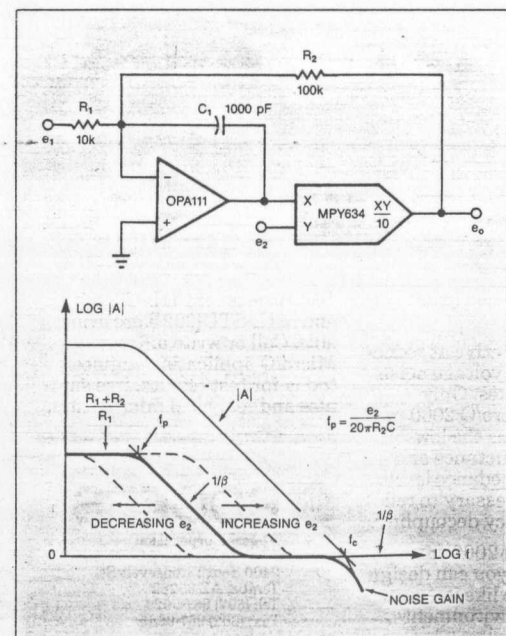


Fig 5—In this filter circuit, variations in the frequency characteristic of  $1/\beta$  make possible a changing  $1/\beta$  slope at the intercept.

frequency end, the composite structure is overridden when  $C_1$  acts as a short circuit, which results in a unity feedback factor around the op amp. This short circuit absorbs all feedback current from  $R_2$  without any corresponding change in the amplifier output voltage. The feedback loop of the composite structure is then disabled, switching feedback control to just the op amp. With  $C_1$  then providing a unity feedback factor to the op amp, the  $1/\beta$  curve follows the unity-gain axis at high frequencies.

Once the  $1/\beta$  levels are fixed at the extremes, the multiplier determines the nature of the transition between the two. In the transition region, feedback currents from  $R_2$  and  $C_1$  compete for control of the summing node of the op-amp input. The contest for dominance is analogous to the frequency-dependent control of impedance with a parallel RC circuit. In both cases, the 3-dB point, where each element carries the same magnitude of current, defines the transition of control. The Fig 5 filter achieves equal element currents when the impedance of  $C_1$  and the effective impedance of  $R_2$  are equal. This equality defines the voltage-controlled roll-off frequency of the filter as previously expressed. At this frequency,  $1/\beta$  also rolls off and drops at  $-20$  dB/decade to the high-frequency limit of the unity-gain axis.

#### What about controlling circuit stability?


The stability conditions of the Fig 5 circuit depend on the particular feedback loop or the combination of elements that are in control at the intercept point. For the lower-frequency filter cutoff frequencies illustrated, the op amp's bypass capacitor takes control before the intercept and defines the relevant feedback conditions. Because the  $1/\beta$  curve follows the unity axis at the upper end, you can guarantee stability by ensuring that the op amp be unity-gain stable. For higher-frequency cutoff frequencies, the  $1/\beta$  transition moves toward the gain-magnitude curve of the op amp. Circuit response cannot move beyond this limit, so the op-amp roll-off becomes the upper boundary of filter operation.

When the cutoff frequency approaches this boundary, the intercept rate-of-closure varies, prompting stability analysis. First, the zero of the  $1/\beta$  curve approaches the intercept, where it increases the slope of the curve. Because this action reduces the rate-of-closure, stability is improved and a more detailed analysis is unnecessary. A continued increase in the cutoff frequency moves the  $1/\beta$  curve further to the

# Looking for a job doesn't have to be one.

EDN's Career Opportunities section keeps you informed of current job openings from coast-to-coast

**TURN TO  
PAGE 248**

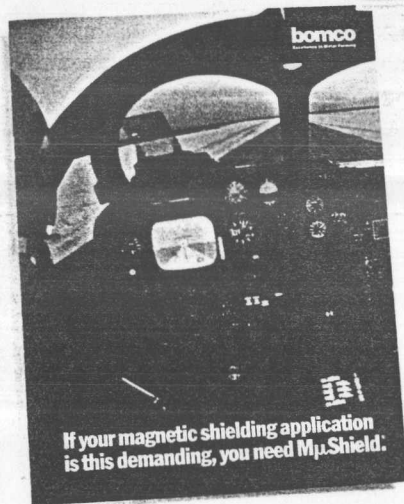

### Free MμShield Magnetic Shielding Catalog

For customized shielding, MμShield materials from stock, and consultation services, contact MμShield Products Division, Bomco, Inc., Route 128, Blackburn Circle, Gloucester, MA 01930. Phone 508/283-9000. Fax 508/283-2882.



CIRCLE NO 65

## "In a hurry?"

Chances are when you need test equipment, you need it immediately. Leasametric delivers—usually within 24 hours.

**Get the best names  
in the business. From  
the best name in the  
business. Leasametric.**  
**1-800-553-2255**



Instrument Rental Division  
1164 Triton Drive  
Foster City, California 94404

**Count on us.**

CIRCLE NO 66

right where its pole interacts at the intercept. This break frequency returns the rate-of-closure to 20 dB/decade, thus retaining stability. Beyond this point, the intercept occurs at the flat lower end of the  $1/\beta$  curve, and no further change in the rate-of-closure takes place.

Utilizing these various feedback conditions and a unity-gain-stable op amp, you can design a composite circuit that fulfills its primary stability requirement over the entire operating range. In addition, however, you may sometimes require a multiplier having a bandwidth much greater than that of the op amp, as the two previous examples demonstrate. Without a wide-bandwidth multiplier,  $1/\beta$  would begin to rise near the higher-frequency intercepts and increase the rate-of-closure. The OPA111 avoids this complication when using the MPY634 multiplier by maintaining a dominant op-amp pole.

Other applications may involve feedback peaking and op amps that are not unity-gain stable—log amps and active filters, for example. For these and other variations requiring feedback analysis, the test remains the same. Look for the critical condition where the rate-of-closure is 40 dB/decade. Where conditions approach this level, conduct further analysis and compare phase-compensation alternatives for optimization.

EDN

### References

1. Graeme, J G, "Designer's guide to op-amp feedback circuits—Part 1," *EDN*, January 19, 1989, pg 131.
2. Lewis, E D, "Compensation of Linear IC Test Loops," *Electronics Test*, May, 1979, pg 83.
3. Dostal, E J, *Operational Amplifiers*, Elsevier Scientific Publishing, Amsterdam, Holland, 1981.
4. Wong, Y, and W Ott, *Function Circuits: Design and Applications*, McGraw-Hill, New York, NY, 1976.
5. Stitt, M, and R Burt, "Möglichkeiten zur Rauschunterdrückung," *Elektronik*, December 1987, pg 112.

### Author's biography

Jerald G Graeme is manager of instrumentation-components design at Burr-Brown Corp (Tucson, AZ), and directs a linear-IC development group. He holds a BSEE from the University of Arizona and an MSEE from Stanford University. Jerry has eight patents to his credit. His leisure pursuits include photography, woodworking, and scuba diving.



Article Interest Quotient (Circle One)  
High 488 Medium 489 Low 490

EDN February 2, 1989

# 500,000 hrs. MTBF

That's acdc. Power Supplies built to keep working, and working, and working! Specifically, our 500 to 1500 watt switchers have MTBF numbers that literally just won't quit.

## INDUSTRY LEADERSHIP

Reliability is designed in first, and verified during the development of each product. Every unit is manufactured with controlled processes, thoroughly computer tested and burned-in at full load (40°C with 60 second AC cycling for up to 48 hrs.), acdc builds supplies like nobody else.

The result is this...exceptionally high MTBF performance demonstrated in the field, setting the new industry standard for reliability.

## GREAT FEATURES... GREAT PRICE!!!

Of course our supplies meet UL, CSA, IEC Safety Specs and can be ordered in any number of output configurations. All this performance for a price you may already be paying for a not-so-reliable brand.

OBSERVED MTBF			
MODELS	POWER	UNITS	MTBF (HOURS)
SINGLES			
RSF501	500W	9,000	877,000
JF751	750W	8,000	448,000
JF101	1000W	11,000	403,000
JF151	1500W	3,000	400,000
MULTIS			
RSF504	500W	8,000	346,000
REV804	800W	10,000	365,000

acdc has maintained a complete database of shipments and returns since 1985. Observed MTBF statistics are calculated per MIL-STD-781.

YOUR  
POWER SUPPLIER  
from 15-2000 watts

**acdc**  
electronics

401 JONES ROAD, OCEANSIDE, CA 92054  
TEL: 619-439-4200 FAX: 619-439-4243

CIRCLE NO 64

